

2

Analog Circuits & Components

2.1> Introduction

Circuit → It is closed path through a series of electronic components in which current flows through.

Electronic Circuit

Analog Circuit

→ Voltage is continuous and can have any value over a specified range.

→ More Sensitive to noise or disturbance than digital.

Digital Circuit

→ Voltage Signal is usually represented by just two different levels (eg 0 & 5 Volt)

→ Small disturbances have no effect.

When Voltage or current varies sinusoidally with time it is called an alternating current (AC) circuit.

2.2> Analog Circuit Elements

Circuit Components

Passive Type


→ Requires no external power to operate.

→ eg: resistors, capacitors


Active type

→ Requires power to operate
→ eg: operational amplifier


Resistors

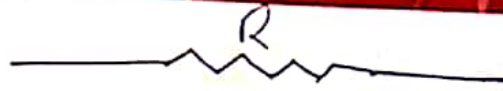

Capacitor

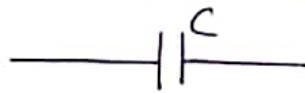

Ideal Voltage Source

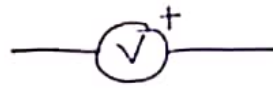


{batteries}

Ideal Current Source




Ideal because they do not have internal resistance, capacitance or inductance

Inductor

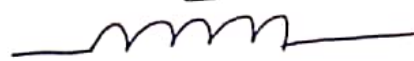


① Resistors

→ Elements that dissipate Energy.

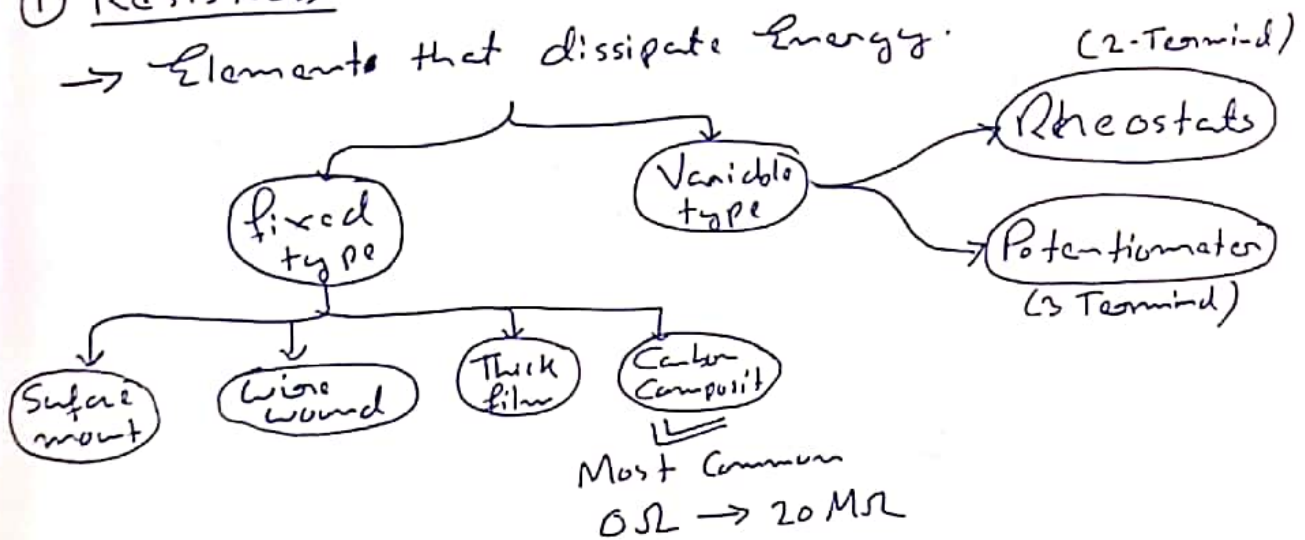

② Capacitors

→ Energy Storing element.

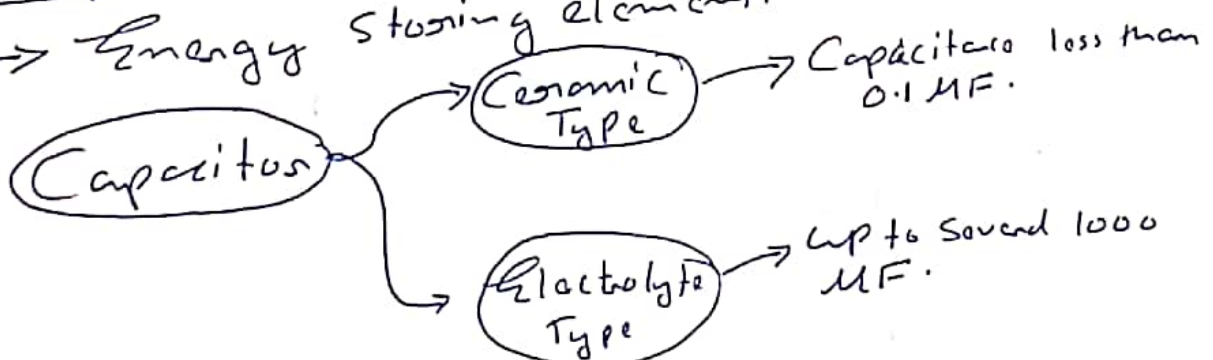


③ Inductors

→ Energy Storing Element.

→ Practically included in Solenoids & motors.

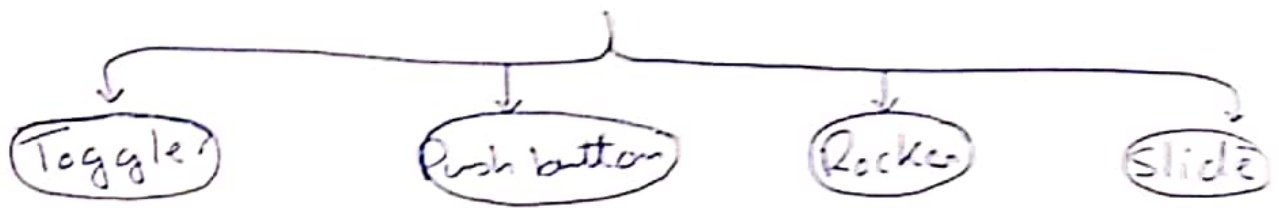23) Mechanical Switch



→ Device that makes or breaks contact in electronic circuit.



⇒ Toggle Switch are specified in terms of their number of poles & throw.


{ No of circuit that can be completed by the same switching action }

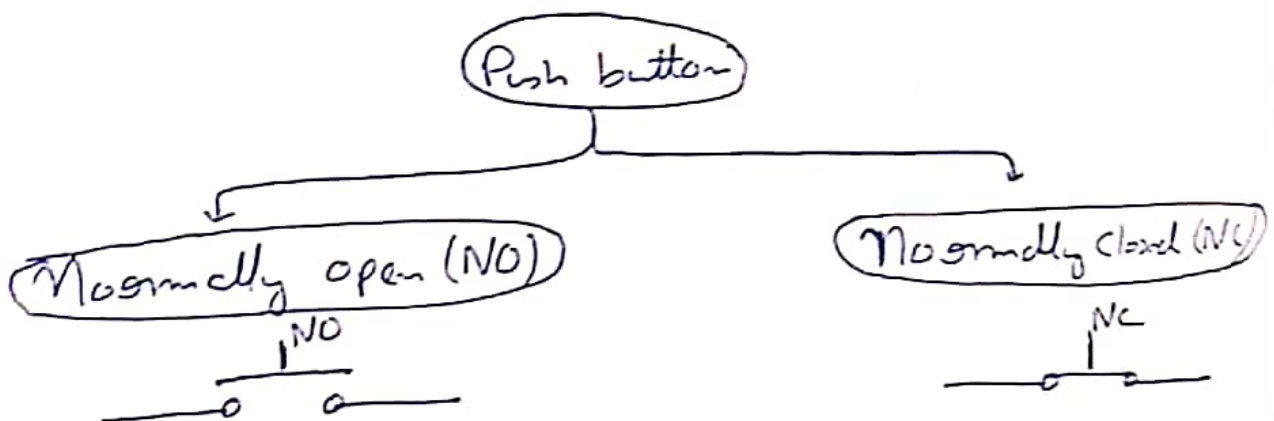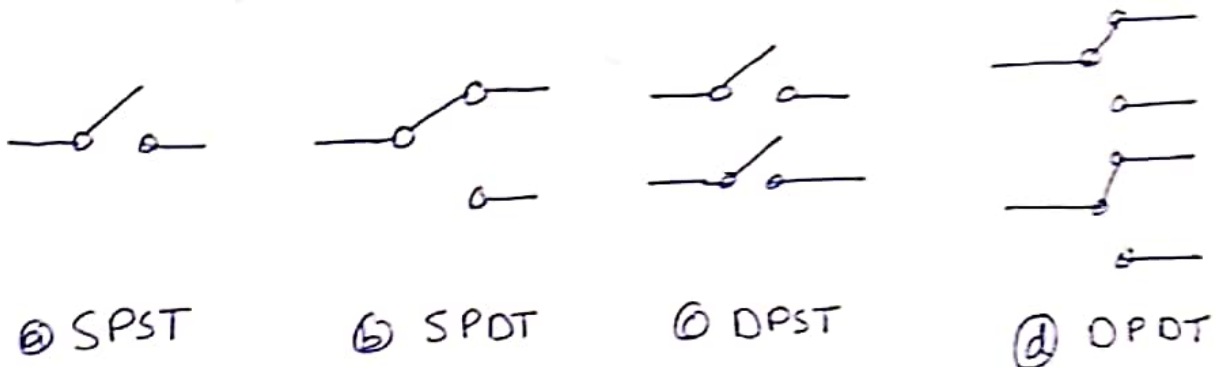{ Number of individual contacts for each pole }



⇒ Push-button Switch are normally used as reset switches or doorbell switch.

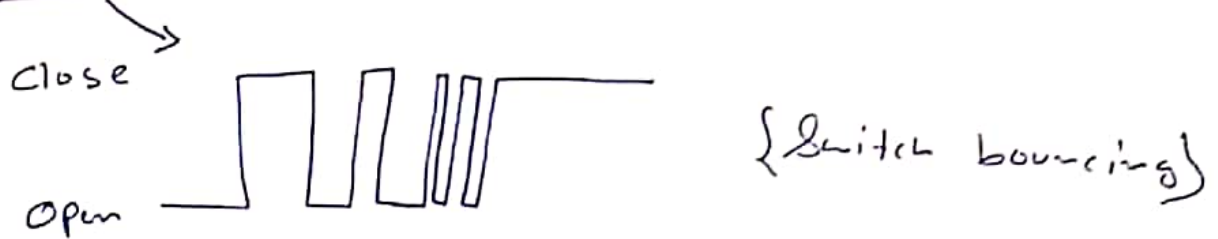One disadvantage of mechanical switches is switch bouncing.




→ The most common approach to solve this problem is to provide for each switch a debouncing circuit that makes use of flip-flop circuit element.

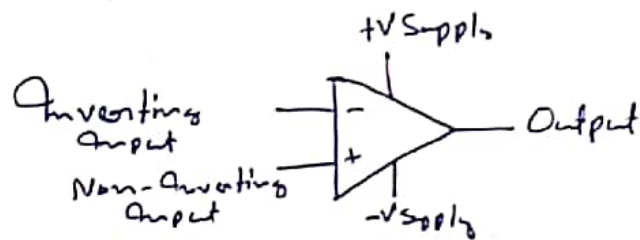2.9) Operational Amplifiers

↳ Active analog circuit component.

→ Widely used is amplification & Signal-Conditioning circuit.




→ There are two other connections to the op-amp (called the balance or null offset) that permit adjustment of the op-amp output, but they are typically not shown.

→ Commercially, op-Amps are available in a variety of forms.

Eg: LM741 (8-pin IC) {National Semiconductor}

→ An op-amp is constructed from a number of components including transistors, diodes, capacitors and resistors.

An ideal op-amp can be modeled as:-

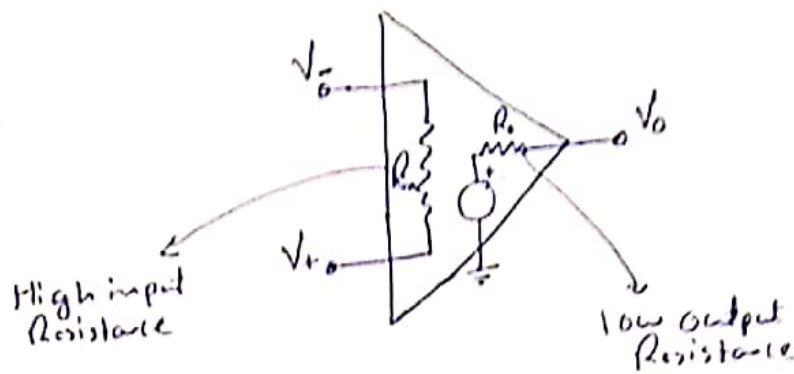

$$V_o = K_{OL} \times (V_+ - V_-)$$


open loop gain
of op-amp

{usually 10^5 to 10^6 }

⇒ Since the op-amp output is finite, but the op-amp has a very large gain, we assume $V_+ = V_-$.

Basis assumptions used to analyze ideal op-amp

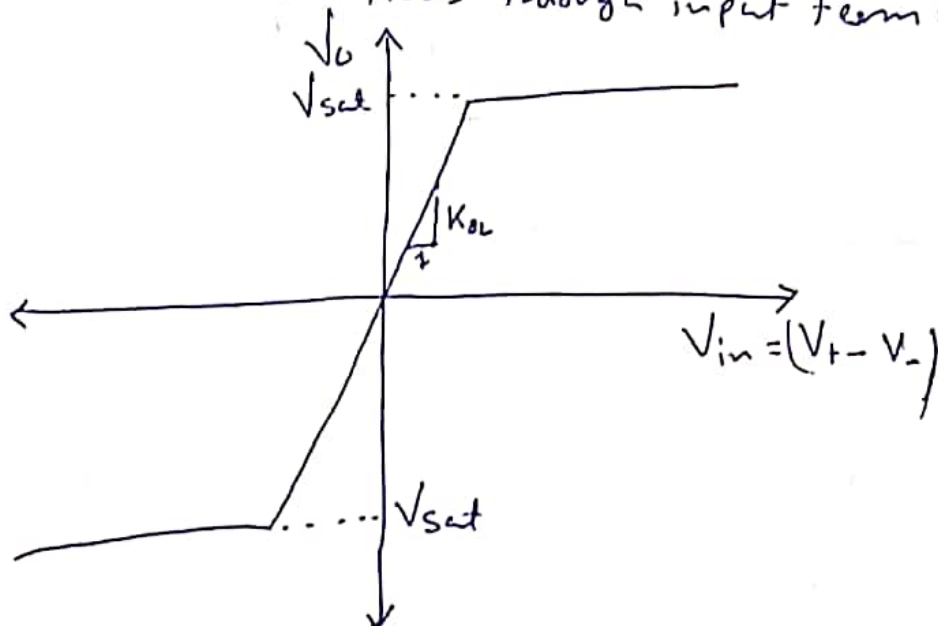- $V_+ = V_-$
- No current flows through input terminals.



Open-loop input/output relationship for an op-amp

⇒ Op-amps have good frequency response characteristic and their bandwidth exceeds 1MHz.

⇒ Op-amps can perform various operations such as:-

i) Comparison

iv) Summation

ii) Amplification

v) Integration

iii) Inversion


vi) Differentiation

vii) filtering


① Comparator Op-Amp

"A Comparator is used to compare two voltage signals, and switch the output to $+V_{set}$ if one of the signals is large than the other, and to $-V_{set}$ otherwise"
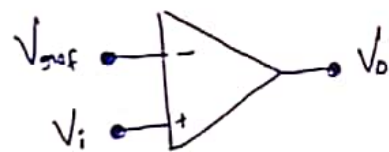
$$V_o = \begin{cases} V_{set} & V_i > V_{ref} \\ -V_{set} & V_i < V_{ref} \end{cases}$$



② Inverting Op-Amp

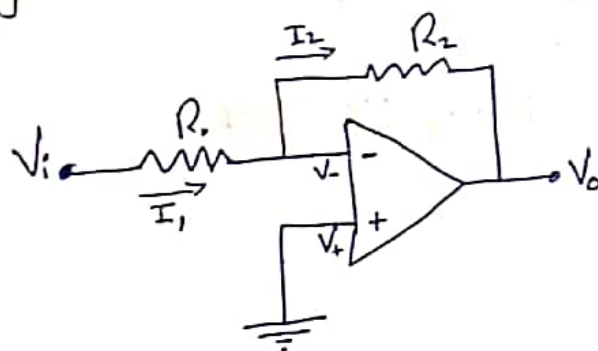

⇒ Since the non-inverting input is connected to ground
 $V_- = V_+ = 0$

⇒ No current flows between the inverting and non-inverting input.

$$I_1 = I_2$$

$$I_1 = \frac{V_i}{R_1}$$


$$I_2 = \frac{-V_o}{R_2}$$

$$\Rightarrow \frac{V_i}{R_1} = \frac{-V_o}{R_2} \Rightarrow \boxed{V_o = -\left(\frac{R_2}{R_1}\right) V_i}$$

\Rightarrow Thus the circuit inverts the input voltage & amplifies it by a factor equal to the ratio of the resistance of R_2 to R_1 .

Application: Signal inversion \Rightarrow Output will have 180° phase shift with the input.

③ Summing Circuit

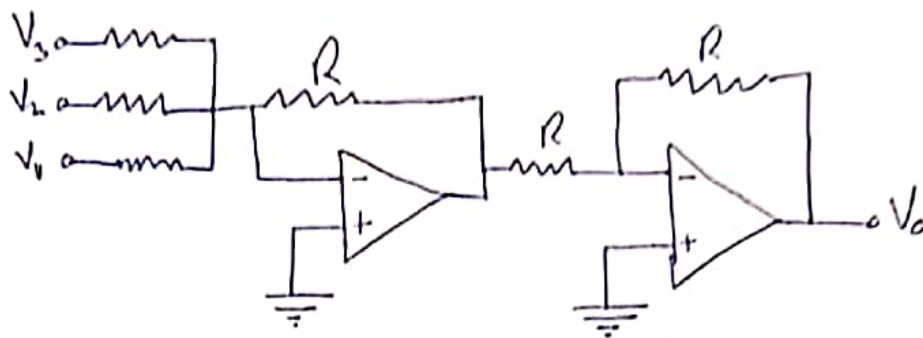

$$\boxed{V_o = V_1 + V_2 + V_3}$$

④ Non inverting Op-Amp


$$\boxed{V_i = V_+ = V_-}$$

$$I_1 = \frac{V_o - V_-}{R_2} = \frac{V_o - V_i}{R_2}$$

$$I_2 = \frac{V_-}{R_1} = \frac{V_i}{R_1}$$

$$\boxed{I_1 = I_2} \Rightarrow \frac{V_o}{R_2} - \frac{V_i}{R_2} = \frac{V_i}{R_1}$$
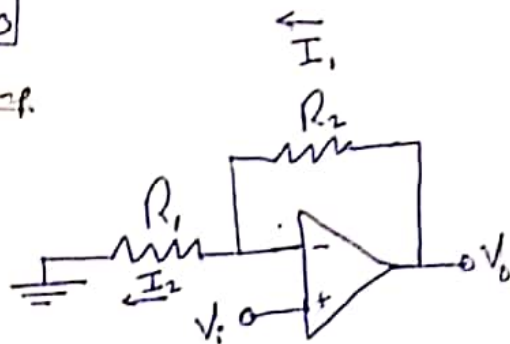
$$V_o = V_i R_2 \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$





⑤


$$V_o = \left(1 + \frac{R_2}{R_1}\right) V_i$$

⇒ This circuit is known as a Voltage follower.

Schmitt trigger

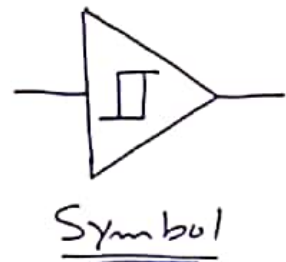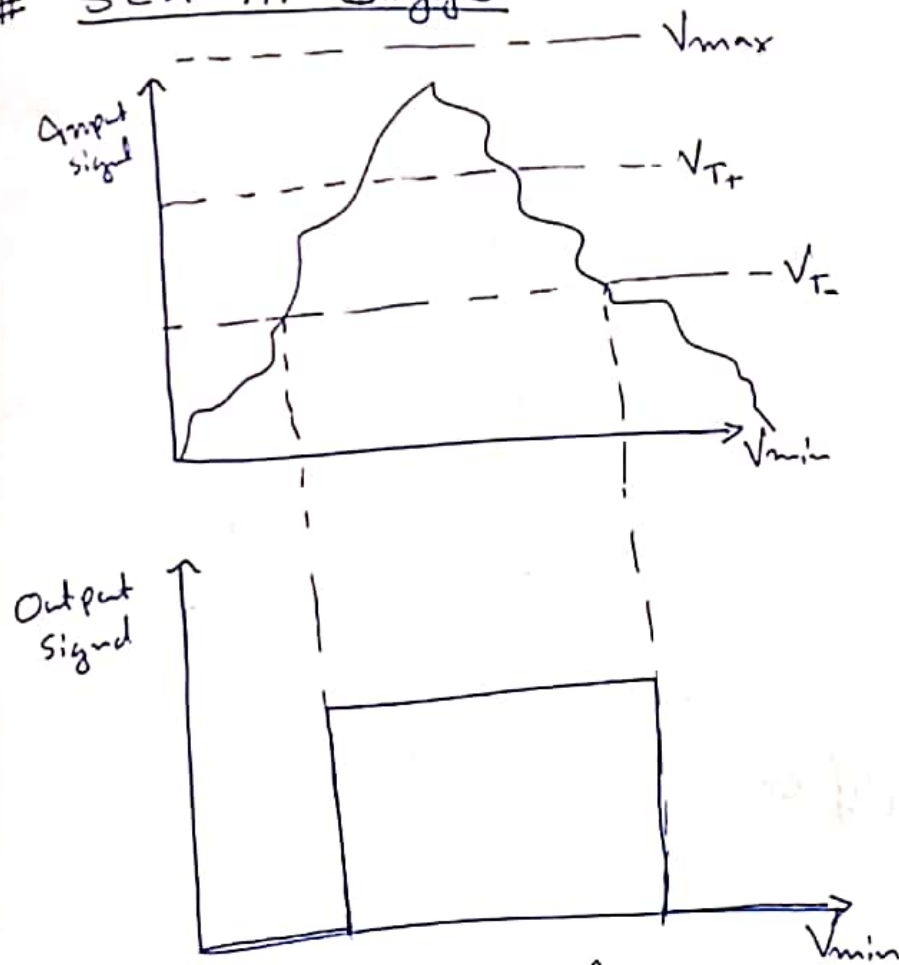


⑤ Differential Op-Amp

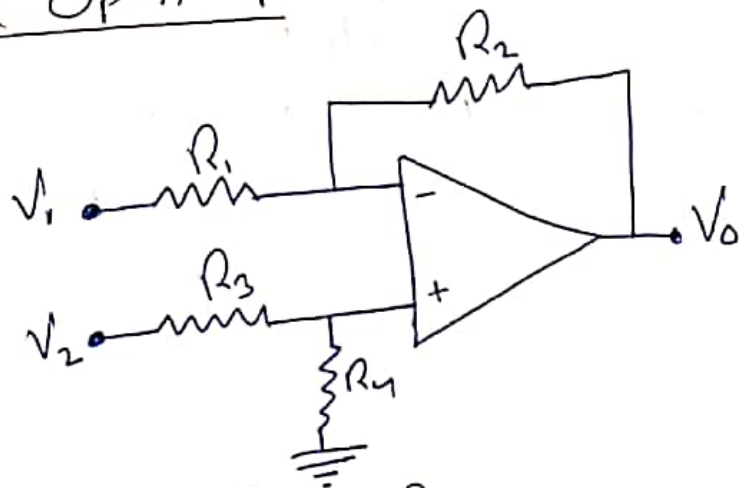

$$V_o = \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_2}{R_1}\right) V_2 - \frac{R_2}{R_1} V_1$$

$$V_o = \frac{R_2}{R_1} (V_2 - V_1) \quad \left\{ \text{Putting } \begin{matrix} R_3 = R_1 \\ R_4 = R_2 \end{matrix} \right\}$$

⑥ Integrating OP-Amp

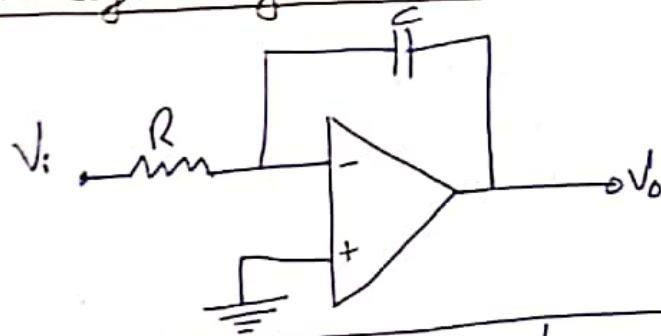

$$\Rightarrow V_o(t) = V_o(0) - \frac{1}{RC} \int_0^{t_i} V_i(t) dt$$

Note: If the Capacitor and the resistor were interchanged in this circuit, the OP-amp will act as differentiator of the input signal.

$$V_o = -RC \frac{dV_i(t)}{dt}$$

⑦ Power Amplifier


(Power op-amp)

→ OP-amp with higher current output rating. ~~and available~~

Eg = OPA547 (by Texas Instruments)

⇒ Due to their large output current, power OP-amp are available in packages with a built in copper tab to allow easy mounting to a heat sink for good thermal performance.

2.10) Grounding

→ Ground Voltage or zero voltage is  commonly used as reference.

2.11) Solenoids & Relays

* Solenoids



→ It is commonly used for on-off applications such as ~~as~~ locking or triggering.

eg ⇒ Electromechanical valves, door locks etc.

→ It is an electrically actuated mechanical device that has two stage:

1) Retracted

2) Extended

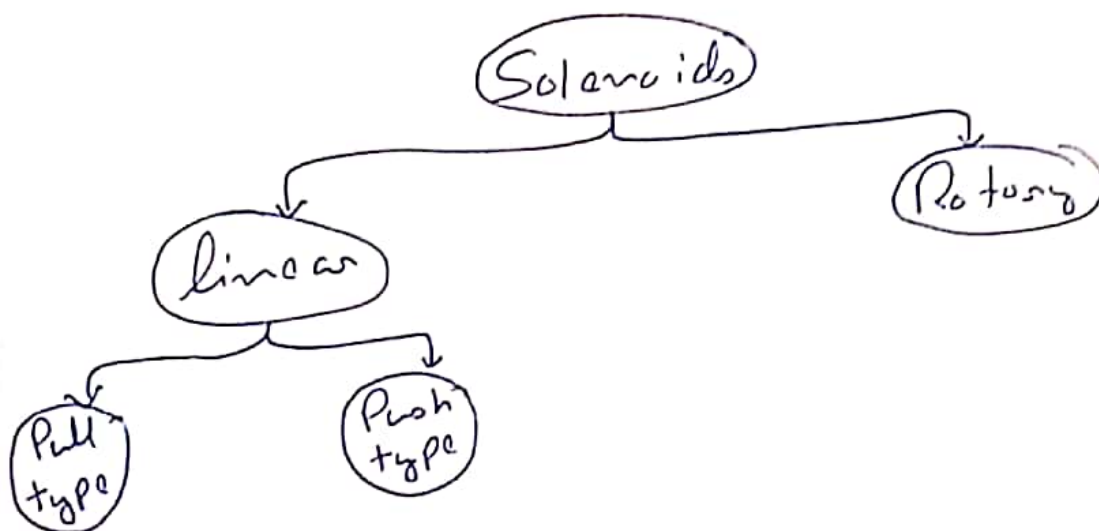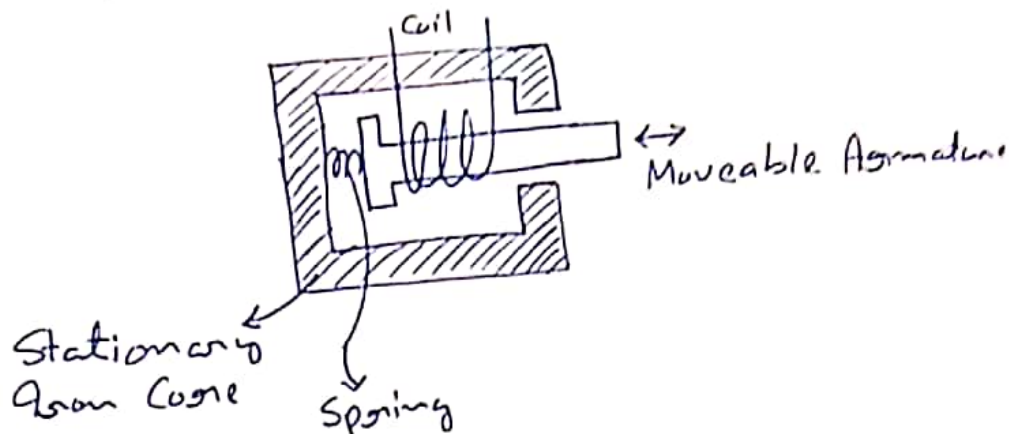

★ Electromechanical Relays

→ Electrically actuated switches that use a solenoid to make or break the mechanical contact between electrical leads.

→ One disadvantage of electromechanical relays is their relatively long switching time.

↳ This is in contrast to solid state transistors, which have nanoseconds switching time.

