

Semiconductor Electronic Devices and Digital Circuit

3.1> Introduction

Semiconductor

→ Materials whose properties are in between a conductor and an insulator.


Eg → Silicon & germanium.

→ For use in semiconductor electronics circuits, small quantity of other elements (such as boron and phosphorus) are added to alter their properties.

→ Their properties depend on temperature, amount & direction of voltage applied to them.

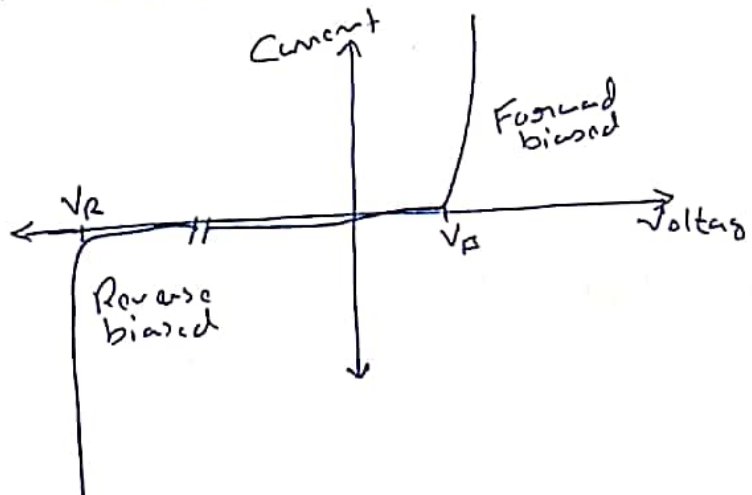3.2> Diodes

A diode is a directional element that allows current to flow in one direction.



For Silicon diode

$$\left\{ \begin{array}{l} V_F = 0.6V \\ V_R = 75V \end{array} \right\}$$

⇒ Regular diodes are not designed to operate with a voltage higher than V_R unless a Zener diode is used

⇒ Uses: → Rectification ($AC \rightarrow DC$)

→ Voltage clamping

→ To limit voltage spikes generated when switching of inductive loads.

★ Zener diode

⇒ It acts as normal diode when it is forward biased but it can conduct current without destroying itself when the reverse-biased voltage exceeds the breakdown voltage V_R .




★ LED (Light emitting diode)

⇒ These diodes emit light when forward biased and amount of light they emit is proportional to the current passing through the LED.



★ Photodiode

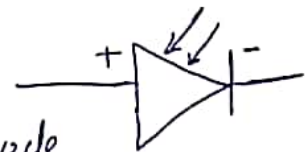⇒ Amount of current that the photodiode passes is proportional to the amount of light it receives, and the current flows from $-$ to $+$ (reverse biased)





⇒ Commonly used as light sensor.

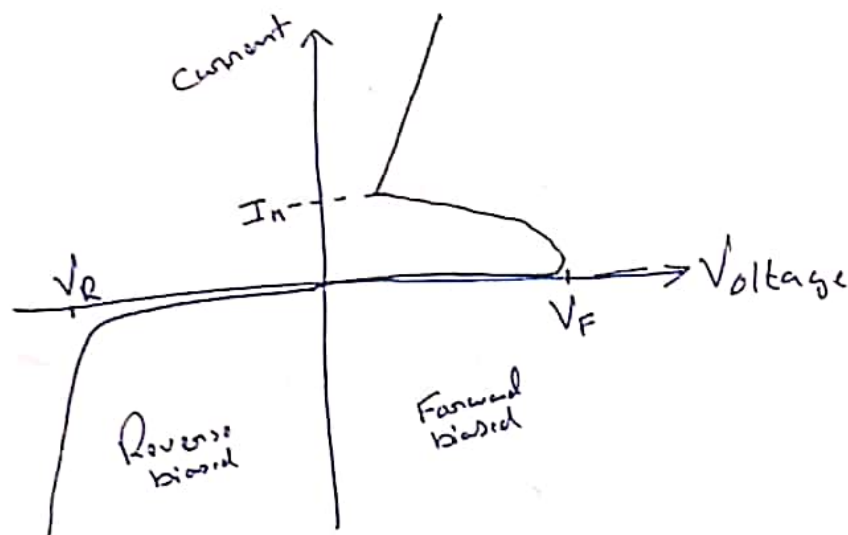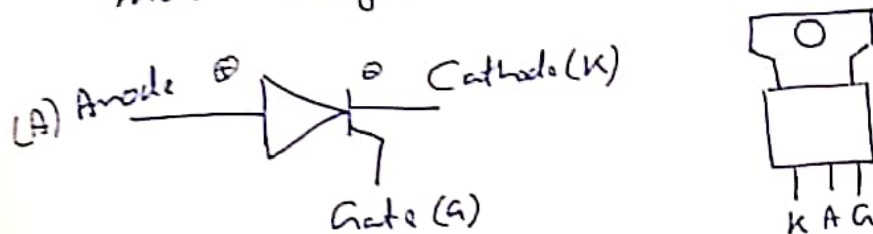3.2) Thyristors

⇒ Three terminal semiconductor device that behaves like a diode but with an additional terminal.

⇒ The additional terminal is called gate, and when small current flows into the gate, it allows a much larger current to flow from ~~the~~ \oplus to \ominus .



⇒ Forward Voltage (V_F) of a thyristor is quite large (50 - Several thousand Volts), unlike regular diode.

⇒ Note: If the current to the gate is cut off, the thyristor continues to conduct as long as the voltage applied causes it to forward bias.

→ Thyristor is turned off only when ~~voltage~~ applied current between the anode & the cathode drops below a certain level. (holding current).



↳ This effect is called Latching.

3.4) Bipolar Junction Transistor

→ Transistor is a Solid-State Switch that opens or closes a circuit.

Switching action is done by change in the electrical characteristics of the device.

→ 3 terminal device.

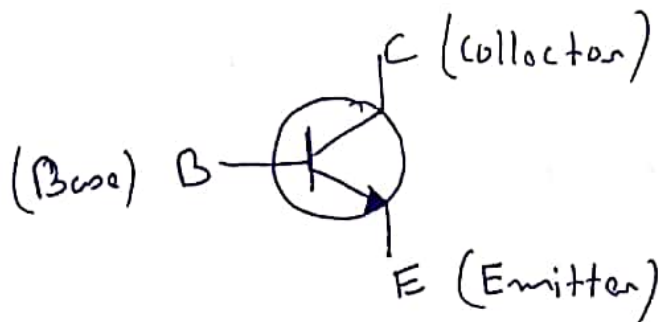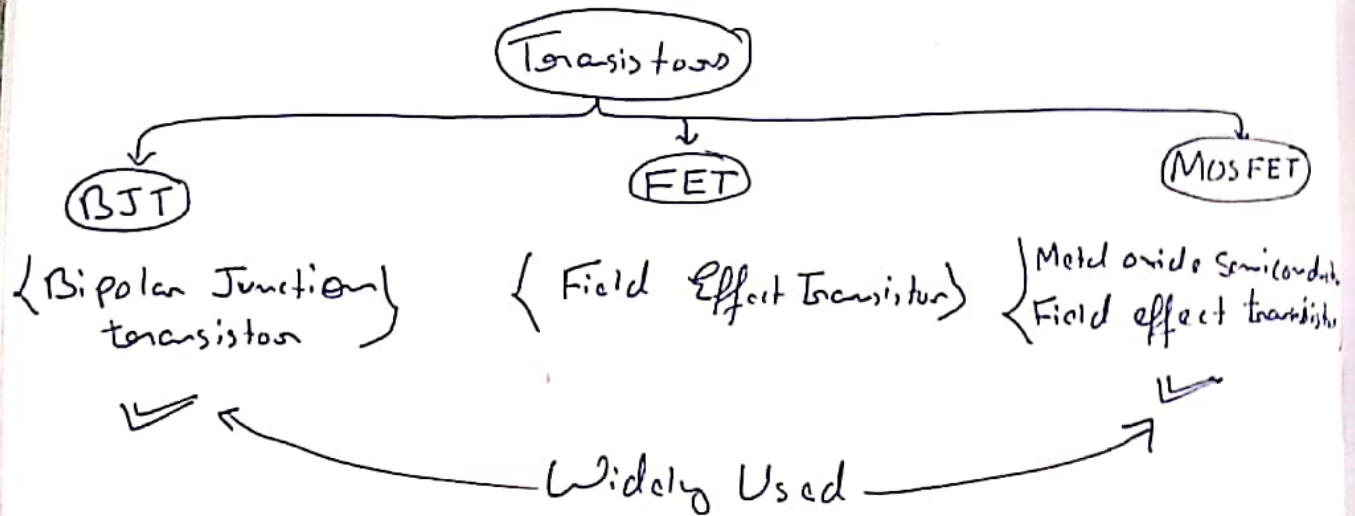

Let us further define:-

$$V_{BE} = V_B - V_E$$

$$V_{CE} = V_C - V_E$$

Some general characteristics of BJT are:-

- BJT is active device.

- BJT is Current-Controlled device whose operation depends on the magnitude of the current supplied to the base.

- Small base current allows a much larger current to flow between collector & emitter.

- BJT has 3 states of operation.

- Non-Conducting State
 - Linear State
 - Saturation state.

⇒ States are set by current supplied to the base.

- Voltage at the emitter is always lower than the voltage at the base by about 0.6V.

- The collector voltage (V_C) has to be more positive than the emitter voltage.


- If AC voltages are applied to the base input, then a DC offset voltage needs to be applied in series to the AC voltage to enable the transistor to be controlled by both the positive & negative part of AC signal.

⇒ Two most Common Standard BJT Circuits are:

① Transistor Switch (Common emitter circuit)

② Emitter follower Circuit


★ Transistor Switch Circuit

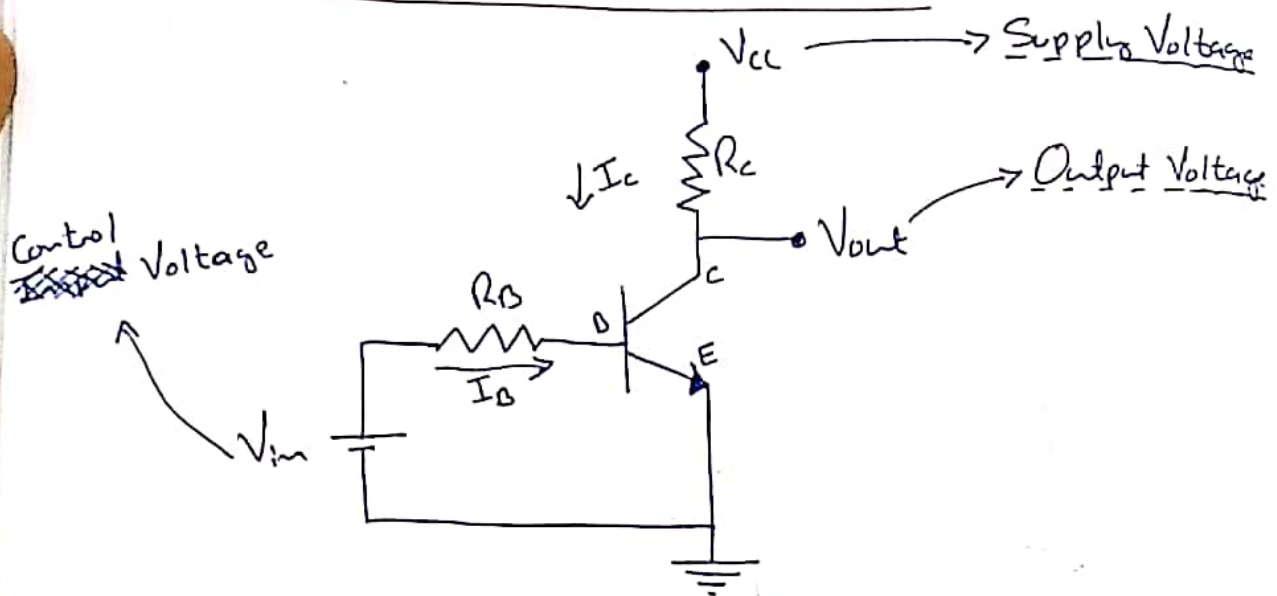

⇒ This Circuit is called Common emitter circuit, because both the emitter & the supply voltage grounds are connected to the same common point

⇒ In practice R_C represents load resistance.

↓
{ This needs to be Switched }
ON & OFF

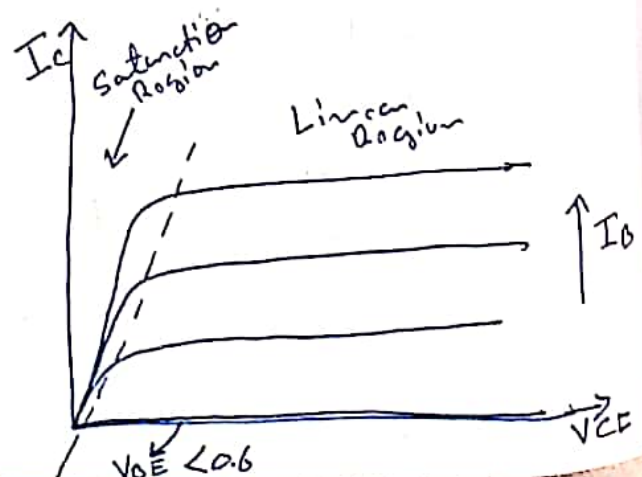

* Off State \Rightarrow When $V_{BE} < \sim 0.6V$

\rightarrow In this state, no current flows between the collector & the emitter ($I_C = 0$).

$$\rightarrow V_{out} = V_{CC}$$

Linear operation state \Rightarrow When $0.7V > V_{BE} \geq 0.6V$
 $[V_{CE} > 0.2V]$

\Rightarrow In the linear operation state, the collector current I_C is linearly related to the base current I_B

$$I_C = \beta I_B = h_{FE} I_B$$

Saturation state $\Rightarrow V_{BE} \geq 0.7V$

\rightarrow Current flows between collector & emitter.

$$\rightarrow V_{CE} = 0.2V$$

$$\rightarrow V_{out} = V_{CE}$$

\Rightarrow In the transistor switch circuit the transistor is normally designed to operate in either the off state or the on state (saturation) state.

\hookrightarrow But not in the linear state.

\Rightarrow The question is what is V_{in} voltage needed to cause the transistor to saturate.

$$V_{in} = I_B R_B + V_{BE} \quad \text{--- (1)}$$

$$I_B = I_C / \beta \quad \text{--- (2)}$$

$$\rightarrow I_C = \frac{(V_{CC} - V_{CE})}{R_C} \quad \text{--- (3)}$$

\therefore (1), (2) & (3) can be used to find V_{in} for saturation.

Example: Voltage Saturation Calculations for the
(2N3904) Transistor

$$R_C = 1\text{k}\Omega \quad R_B = 5\text{k}\Omega, \quad V_{CC} = 10\text{V}$$

From data sheet $V_{CE} = 0.2\text{V}$ at saturation
 ~~$I_C = 10\text{mA}$~~

$$\text{So } I_C = \frac{V_{CC} - V_{CE}}{R_C} = \frac{10 - 0.2}{1000} = 9.8\text{mA}$$

$$I_{C,\text{max}} = 200\text{mA}$$

$$h_{FE} = \beta = 100$$

$$V_{BE} > 0.65\text{V} \text{ for saturation}$$

$$\text{We set } V_{BE} = 0.7\text{V}$$

$$I_B = I_C / \beta = \frac{9.8}{100} = 0.098\text{mA}$$


$$\begin{aligned} V_{in} &= (I_B R_B) + V_{BE} \\ &= (0.098 \times 10^{-3} \times 5 \times 10^3) + 0.7 \\ &= 1.19\text{V} \end{aligned}$$

\Rightarrow To insure saturation V_{in} has to be greater than 1.19V .

\hookrightarrow This can be achieved easily if we let $V_{in} = 2\text{V}$ (for example)

\Rightarrow When transistor is off, V_{in} has to be less than V_{BE} .

★ Emitter Follower Circuit

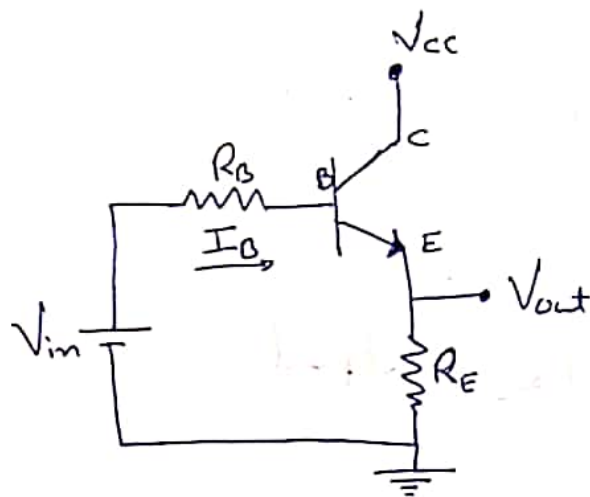

⇒ This circuit is called the emitter follower, because the output voltage follows the input voltage with a difference of about 0.6 V.

$$V_{out} = V_{in} - I_B R_B - V_{BE}$$

$$\boxed{V_{out} = V_{in} - I_B R_B - 0.6} \quad \{ \text{if } V_{in} > 0.6 \text{ V} \}$$

$$\boxed{I_E = I_C + I_B}$$

$$\boxed{I_E = \frac{V_{out}}{R_E}}$$

$$\boxed{I_C = \beta I_B}$$

$$\Rightarrow \boxed{I_B = \frac{I_E}{1 + \beta} = \frac{V_{out}}{(1 + \beta) R_E}}$$

$$\boxed{V_{out} = (V_{in} - 0.6) \frac{(1 + \beta) R_E}{R_B + (1 + \beta) R_E}}$$

→ Output is independent of supply voltage

⇒ The above equation is valid as long as transistor is not saturated.

⇒ When transistor is saturated $\boxed{V_{out} = V_{cc} - 0.2}$

⇒ BJT transistors have certain parameters that should not be exceeded.


- Maximum Collector Current
- Power dissipation Capability.

→ BJT is typically used for low-power applications.

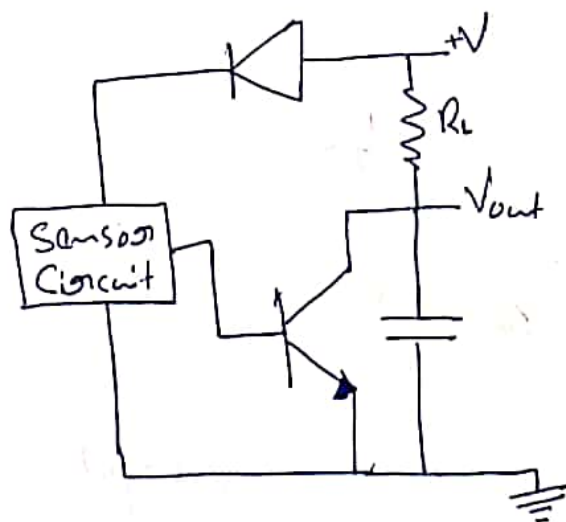3.4.3) Open Collector Output

⇒ Many sensors used in mechatronic applications, such as proximity sensor, have electronic circuits that use an internal BJT transistor as interface.

⇒ To get an output from these sensors, an appropriate "pull-up" resistor or load and the supply voltage needs to be applied to the terminals of the sensor.



⇒ When the proximity sensor is off, the transistor is not in saturation, and there will be no voltage drop across load.

$$V_{out} = V$$

⇒ When an object is detected by the proximity sensor, the transistor conducts and a voltage drop develops across the load resistance.

3.4.4) Phototransistor, Photo Interrupter & Opto-Isolator

Phototransistor

⇒ Instead of using a voltage source to saturate the transistor, a phototransistor uses light to do the same thing.

⇒ Typically a phototransistor and LED are packaged together to make optical sensors that can detect the presence of object called Photo interrupters.

⇒ Opto-isolator / Optocoupler combines two elements similar to a photo interrupter but in an enclosed package.

3.5) Metal-Oxide Semiconductor Field Effect Transistor


→ They are also 3-terminal devices as BJT but they have different names for the terminals, and they operate differently.

Three terminals

- Gate (Similar to base)
- Drain (Similar to collector)
- Source (Similar to emitter)

⇒ Naming of the terminal comes from the flow of electrons between the source & drain when the transistor is conducting.

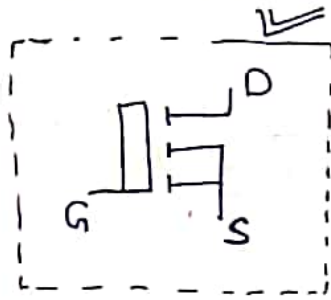⇒ The most commonly used MOSFET is the enhanced type and is available as n-or p type.



⇒ MOSFETs have the following characteristics:-

- The voltage applied to the gate is the signal that controls the operation of the transistor and hence the name field effect transistor.

↳ This is in contrast to a BJT where the current applied to the base controls its operation.

- The gate is insulated from the drain-source circuit. (Indicated in the symbol)

↳ The gate has a high internal resistance ($R_{gate} = 10^{14} \Omega$)

↳ Almost no current flows through the gate. (leakage current in nanoampere range)

↳ This high impedance of mosfet gives it an advantage in interfacing with other logic circuit.


- Mosfet have three States:

- 1) Cutoff
- 2) active
- 3) Saturation

- They act as Voltage-Controlled resistors.

↳ when off, drain source resistance is very high
 ↳ when fully on, drain source resistance is very low
 ↳ Current flows from drain to source.

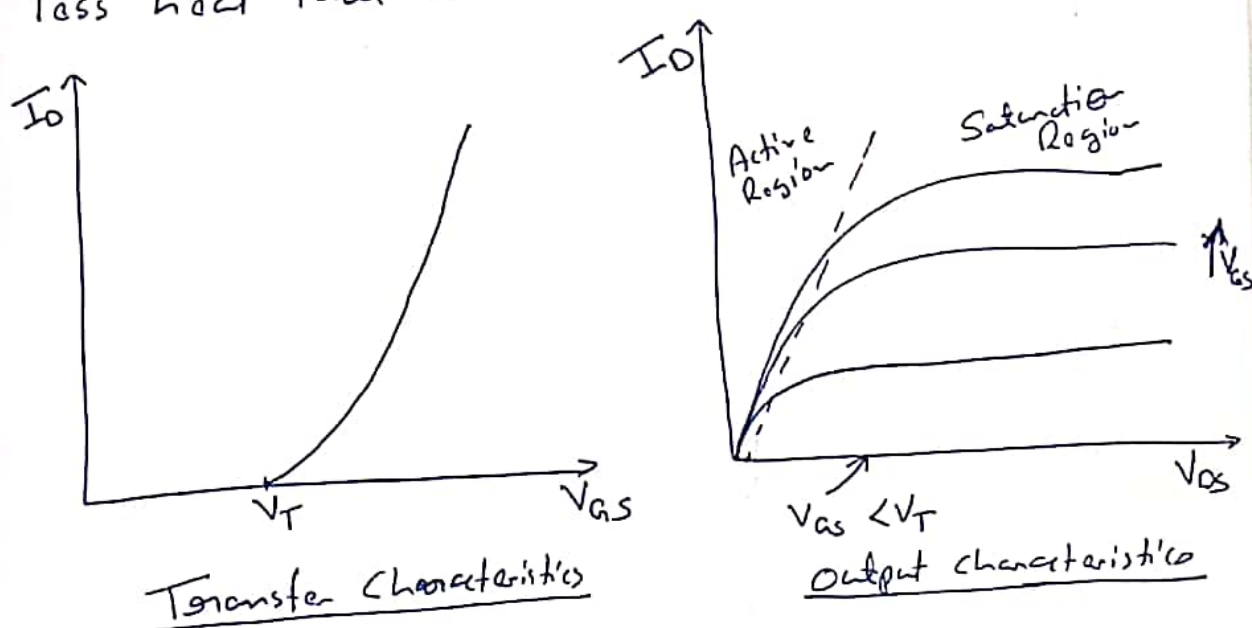- n -type enhancement Mosfet operates with a positive voltage applied to the gate.
- MOSFETs have higher power rating & generate less heat than BJTs.




→ V_T is between 2V to 5V.

⇒ MOSFETs are typically used for switching applications (ON/OFF) to drive motors or LED.


⇒ Mosfets are mounted on heat sink.

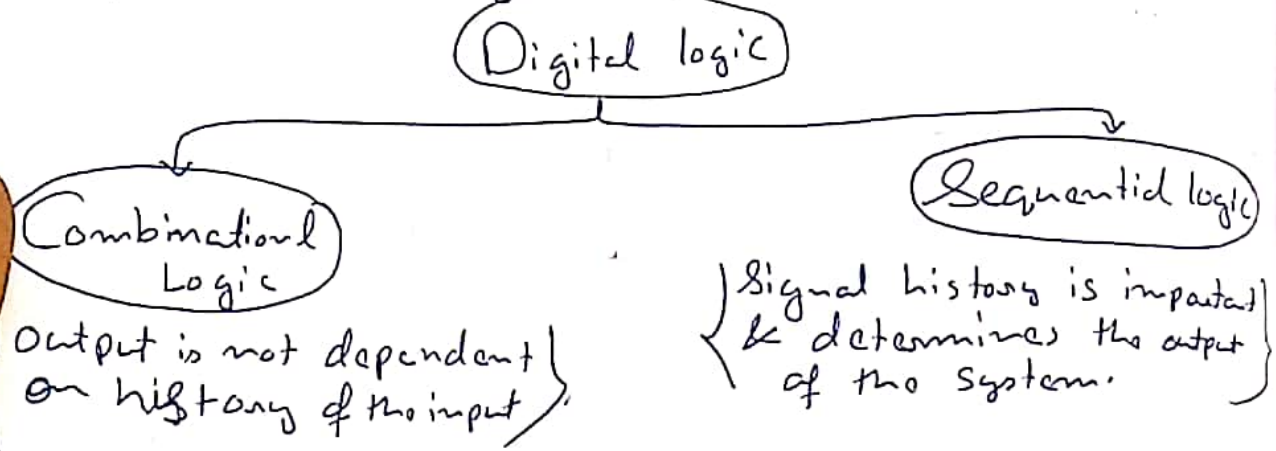
3.6) Combinational Logic Circuit

⇒ The invention of the transistor had led to the development of digital circuits in which transistors form the building blocks.



Basic Combinational logic devices:-

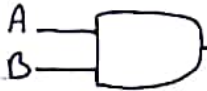
① AND gate →  → $C = A \cdot B$

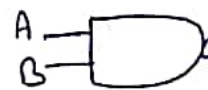
② NAND Gate →  → $C = \overline{A \cdot B}$

③ OR Gate →  → $C = A + B$

④ NOR Gate →  → $C = \overline{A + B}$

⑤ XOR Gate →  → $C = A \oplus B$

⑥ Buffer →  → $C = A$

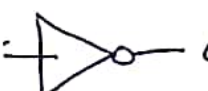⑦ Inverter →  → $C = \overline{A}$

★ Boolean Algebra

↳ Rules governing operations of binary variables.

$$① A + A = A$$

$$② A + 1 = 1$$

$$③ A + 0 = A$$

$$④ A \cdot A = A$$

$$⑤ A + B = B + A$$

$$⑥ A \cdot (B + C) = AB + AC$$

$$⑦ A + (B \cdot C) = (A + B) \cdot (A + C)$$

$$⑧ A + \bar{A} = 1$$

$$⑨ A \cdot \bar{A} = 0$$

$$⑩ A \cdot 0 = 0$$

$$⑪ A \cdot 1 = A$$

$$⑫ \overline{A + B + C + \dots} = \bar{A} \cdot \bar{B} \cdot \bar{C} \dots$$

$$⑬ \overline{A \cdot B \cdot C \dots} = \bar{A} + \bar{B} + \bar{C} + \dots$$

De Morgan rules

★ Boolean Function generation from true table

"Here we look at problem of finding a logic gate system with the minimum number of gates that can be used to realize a logic circuit operation that is specified in terms of a true table"

⇒ The basic approach is to manipulate the logic function into one of two equivalent forms:-

① Sum of product forms: \swarrow {More commonly used}
 $AB + AC$


② Product of sums form:
 $(A+B) \cdot (A+C)$

⇒ Karnaugh map is a graphical method that can be used to produce simplified Boolean expressions from sum of product obtained from true table.

★ Multiplexers & Decoders

Multiplexer

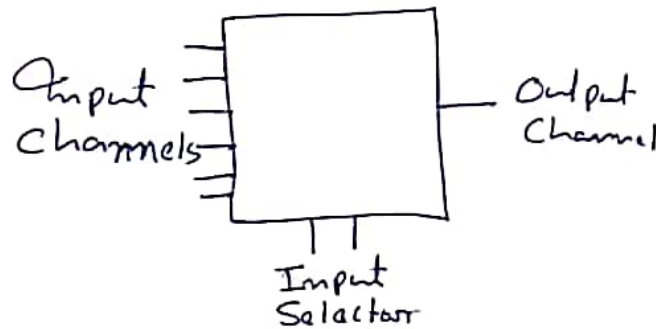→ Circuit that selects one input out of the several available to be connected to the output.



→ Commonly used in the design of ADC Converter & in microcontroller circuit to select the timing source.

→ Multiplexer with 2^n input channels need n channel selector input.

Decoders or Demultiplexer

→ A decoder with n input & m outputs will activate only one of the m output for a specified pattern of the n inputs.

→ operate in opposite fashion to a multiplexer.

3.7 > Sequential Logic Circuit

⇒ Sequential logic can be thought of as Combination logic circuit and memory.


flip-flop ⇒ A Sequential logic device that can store and switch between two binary states.

eg of other sequential logic circuit ⇒ Counter, Shift register & microprocessors.

Flip-flop


- SR
- Clocked SR
- JK
- D
- T

★ SR Flip flop

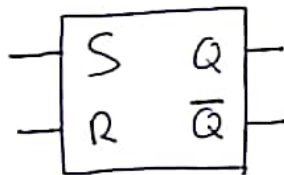

Operation

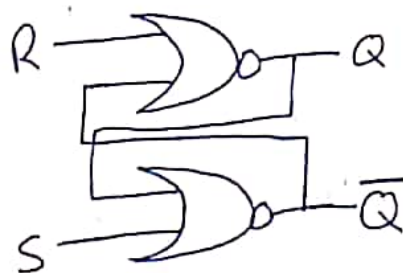- ① $S=0$ & $R=0$ ⇒ Output of flip-flop does not change.
- ② $S=1$ & $R=0$ ⇒ flip-flop is set to $Q=1$ & $\bar{Q}=0$
- ③ $S=0$ & $R=1$ ⇒ flip-flop is reset to $Q=0$ & $\bar{Q}=1$
- ④ S & R are not allowed to be 1 simultaneously, since the output will not be predictable.




{ Equivalent circuit }

★ Clocked SR Flip-Flop

Clock signal

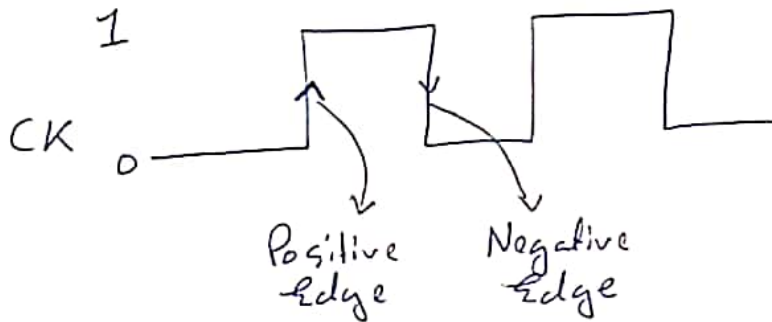- Two stage signal
- Generally square & periodic but can be non-periodic



Positive edge trigger device


Negative edge trigger device

"Responds to low to high"


"Responds to high to low"

⇒ In a clocked SR flip-flop, the output changes state at clock transition.

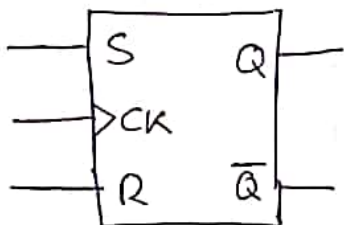↳ This is done to provide Synchronization of the output change in complex system.



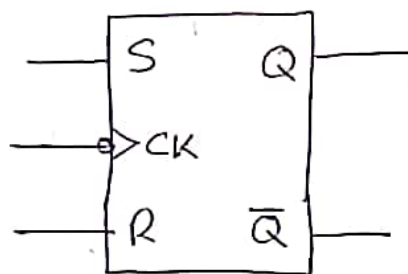
Positive edge triggered
clocked SR flip flop



Negative edge triggered
clocked SR flip flop

★ JK Flip flop

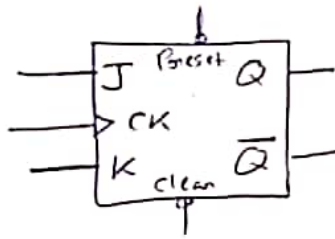⇒ A JK flip flop is similar to an SR flip-flop, but allows a simultaneous input $J=1$ & $K=1$.




⇒ Preset input sets the output Q to 1 & Clear input sets the output Q to zero.

⇒ $J=1$, $K=1$ & $CK=1$ ⇒ ~~No state change~~ Output flips

★ D Flip Flop (Data flip flop)

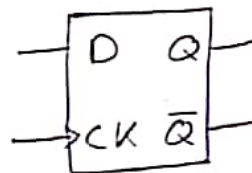⇒ Typically used to represent data registers.




Set of memory elements that are used to hold information until it is needed

Latch → { Similar to D flip flop but its clock input is not edge triggered }
→ Commonly used to maintain the output in DAC.

★ T Flip flop

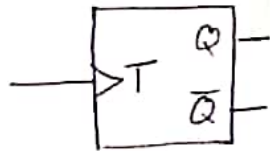⇒ If J & K input of the flip-flop are permanently set to 1 and the input is applied at the clock input, we get what is called T or Toggle flip flop.




⇒ A characteristic of the T flip flop is that the output changes its state at a frequency that is half of the input clock frequency.

↳ This feature is utilized in the construction of
 → Binary Counter
 → Frequency divider.

⇒ It is very important in digital circuits to reduce the noise in the power supplied to the circuit.

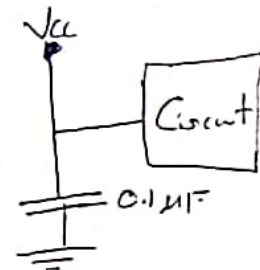↳ This can be done by bypass capacitor as shown.



(Purpose)

↳ To dampen AC Component in the DC signal

3.8) Circuit Families (Digital)

TTL

Transistor-Transistor Logic

↳ Based on BJT Technology

CMOS

Complementary metal-oxide Semiconductor

↳ based on FET Technology


TTL & CMOS Voltage Levels

Operations	Low State Voltage Range		High state Voltage Range	
	TTL	CMOS	TTL	CMOS
Input	0-0.8V	0-1.5V	2.0-5V	3.5-5V
Output	0-0.5V	0-0.05V	2.7-5V	4.95-5V

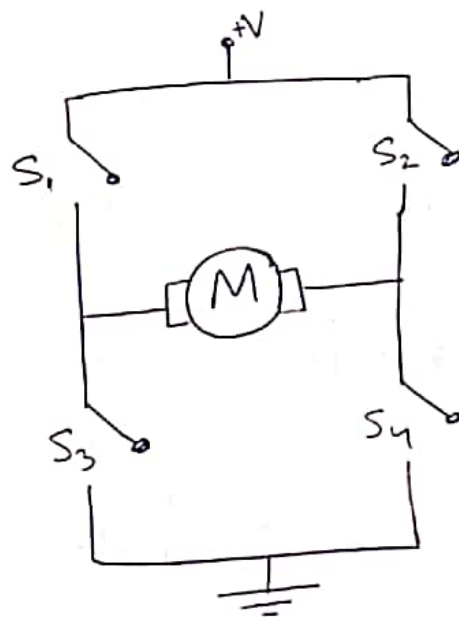3.9 > H-Bridge driver

→ A very common application of transistors is to construct drivers to drive motors.

↳ One such circuit is H-bridge drive circuit.



⇒ Switching elements used are transistors.

↳ Transistor can be BJT or MOSFET depending upon power requirement.